
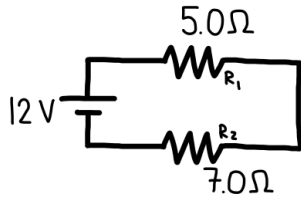


For each circuit, determine the voltage, current and resistance through each resistor and the total voltage, current and resistance of the circuit.


1.

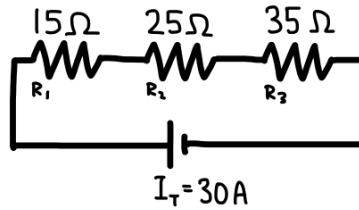


2.




3.

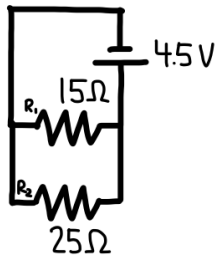


4.

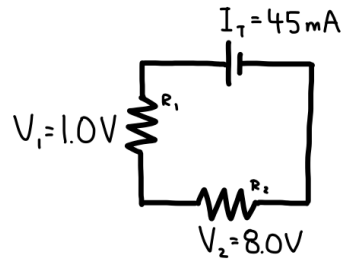


5.

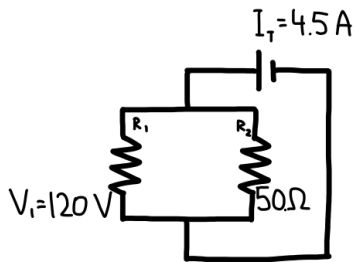

6.

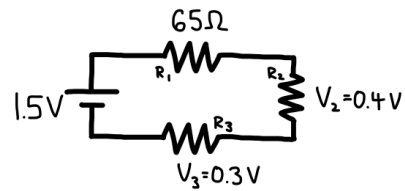

7.

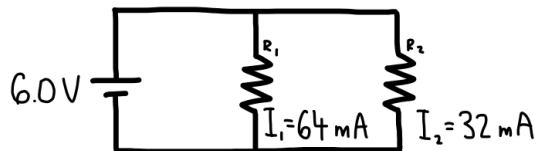

8.

